

*Heaven's light is our guide.*

# Rajshahi University of Engineering and Technology (RUET)

Department of Electrical & Electronic Engineering

**Course no.**      EEE2204

**Course title:**      Electronics III Sessional

**Experiment no.**      04

**Experiment name:** Experimental study of a comparator and a Zero crossing detector circuit using Op-Amp.

**Submitted to:**

**Dr. Md. Samiul Habib**

Associate Professor

Dept. of Electrical & Electronic Engineering,

Rajshahi University of Engineering and Technology.

**Submitted by:**

**Ashraf Al- Khalique**

**Roll: 1801171; Session: 2018-2019**

Dept. of Electrical & Electronic Engineering,

Rajshahi University of Engineering and Technology.

**Date of experiment:**      March 18, 2021.

**Date of submission:**      March 24, 2021.

## Experiment no. 04

**Name of the Experiment:** Experimental study of a comparator and a Zero crossing detector circuit using Op-Amp.


**Objectives:** Followings are the main objectives of this experiment,

1. To understand the theory of operation of a comparator and a Zero crossing detector circuit.
2. To study the Op-Amp applications in a comparator and a Zero crossing detector circuit.
3. To observe wave shapes that meet a comparator and a Zero crossing detector circuits' needs.


### List of Components:

1. Function Generator
2. DC power supply (61mV)
3. Resistors (1k $\Omega$ ; 1 piece)
4. Op-Amp ( $\mu$ A741; 1 piece)
5. Oscilloscope
6. Project board
7. Connecting wires
8. Simulator (Multisim 11.0)

### Circuit diagram:

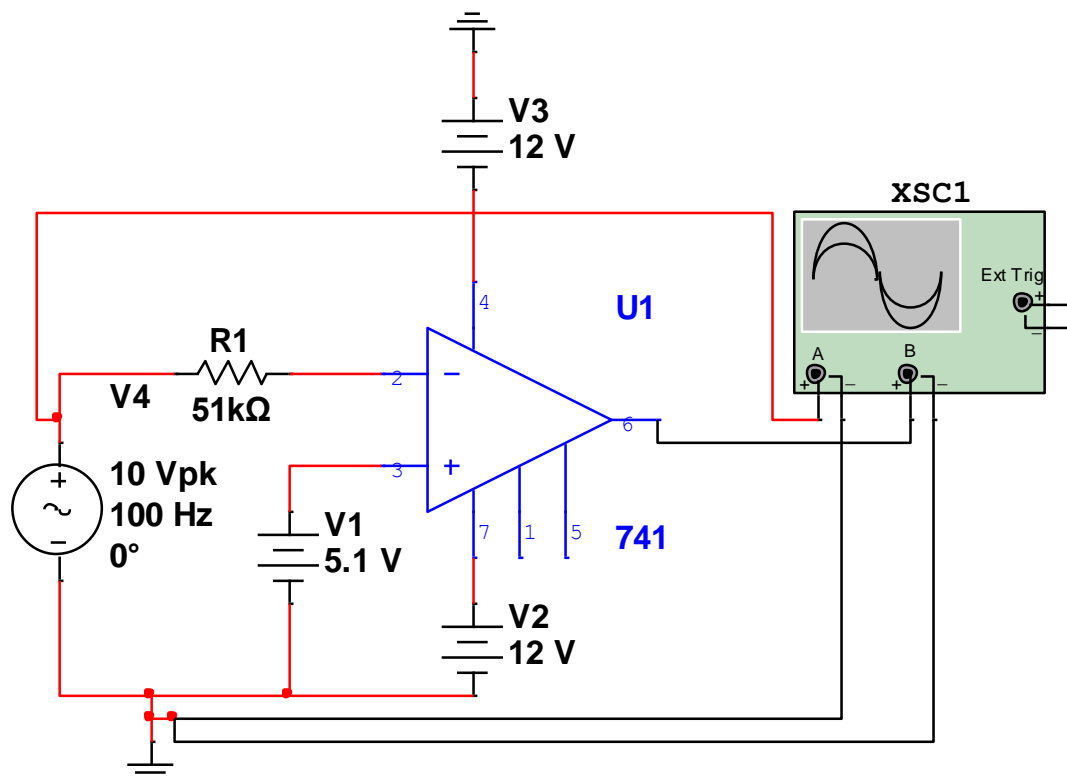


*Fig 1.1: Circuit diagram for a comparator circuit using Op-Amp.*

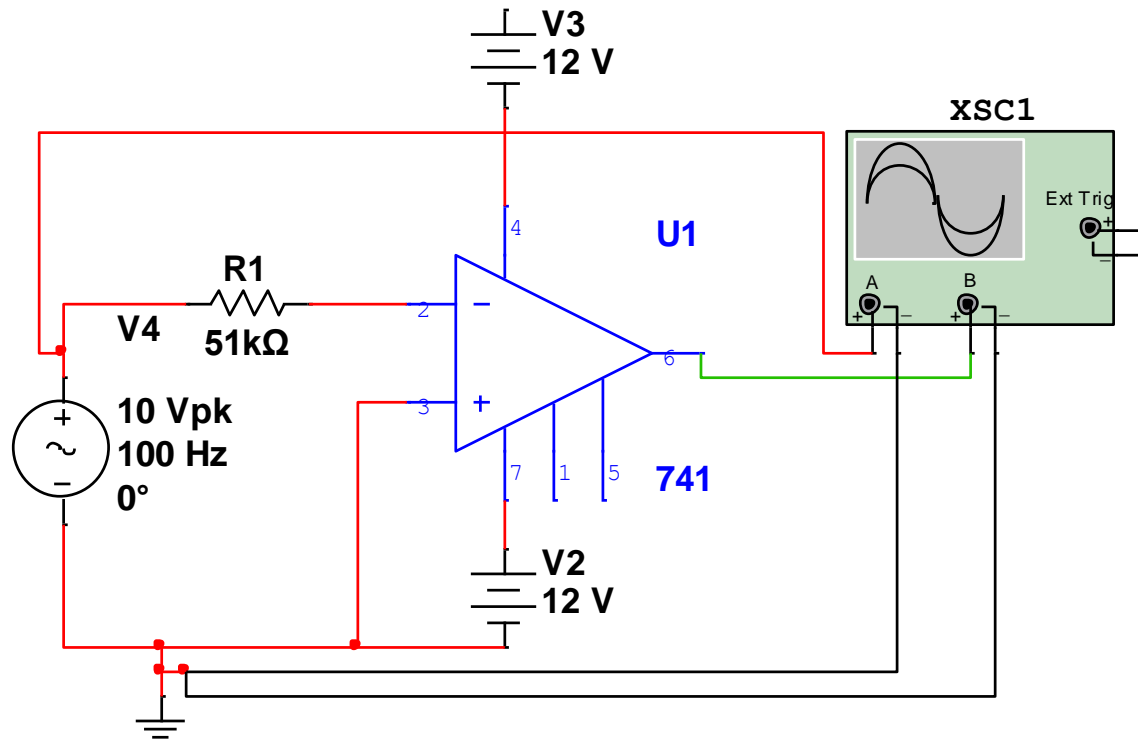


*Fig 1.2: Circuit diagram for zero-crossing detector circuits using Op-Amp.*

**Waveshape:**


**1. Comparator circuit using Op-Amp:**

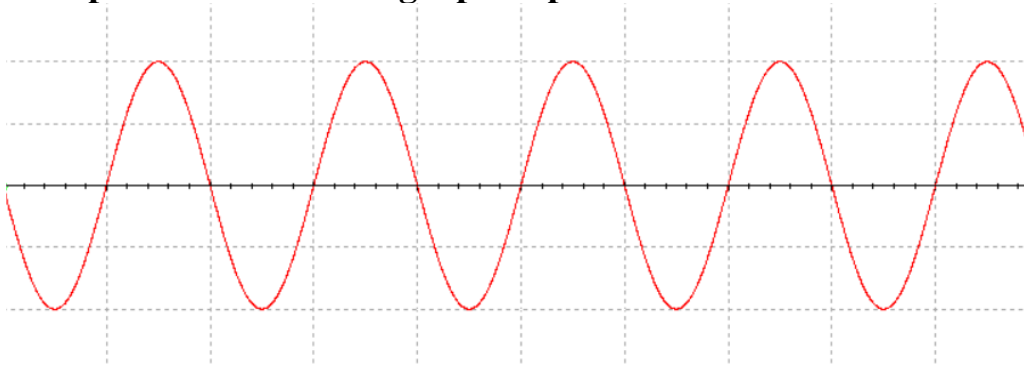


*Graph 1.1: Input signal for a comparator circuit using Op-Amp.*

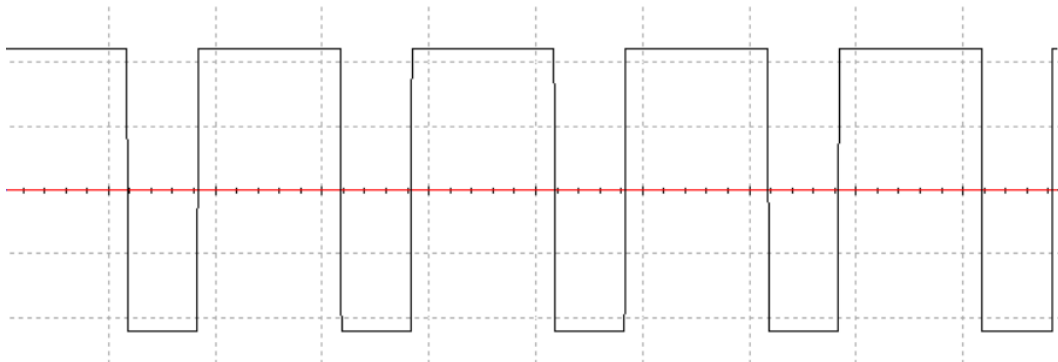

*Graph 1.2: Output signal for a comparator circuit using Op-Amp.*

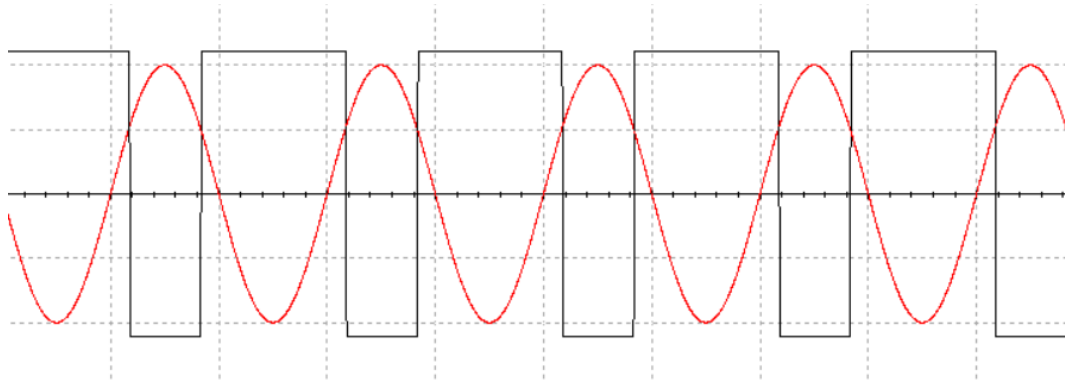

**Graph 1.3:** Input and output signal for a comparator circuit using Op-Amp.

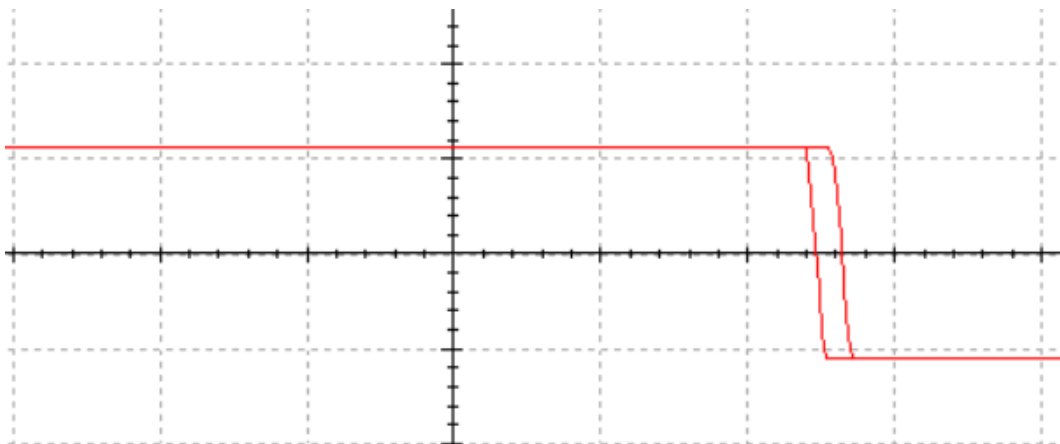


**Graph 1.4:** Transfer characteristics for a comparator circuit using Op-Amp.


## 2. Zero crossing detector circuits using Op-Amp:




**Graph 2.1:** Input signal for zero-crossing detector circuits using Op-Amp.

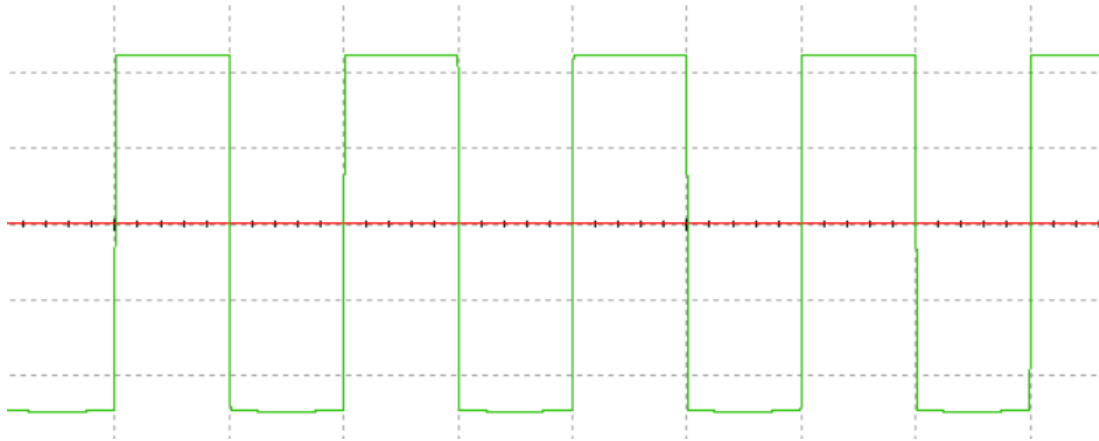

**Graph 2.2:** Output signal for zero-crossing detector circuit using Op-Amp.

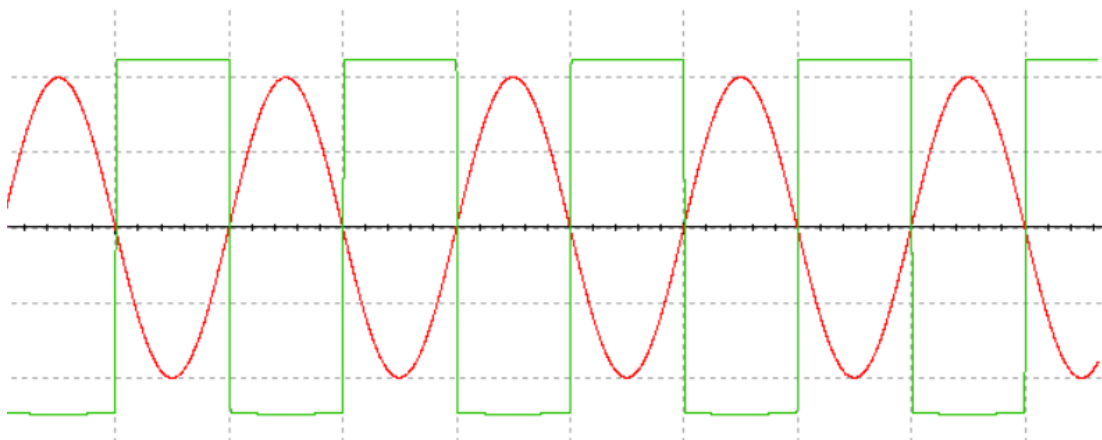

**Graph 2.3:** Input and output signal for zero-crossing detector circuits using Op-Amp.

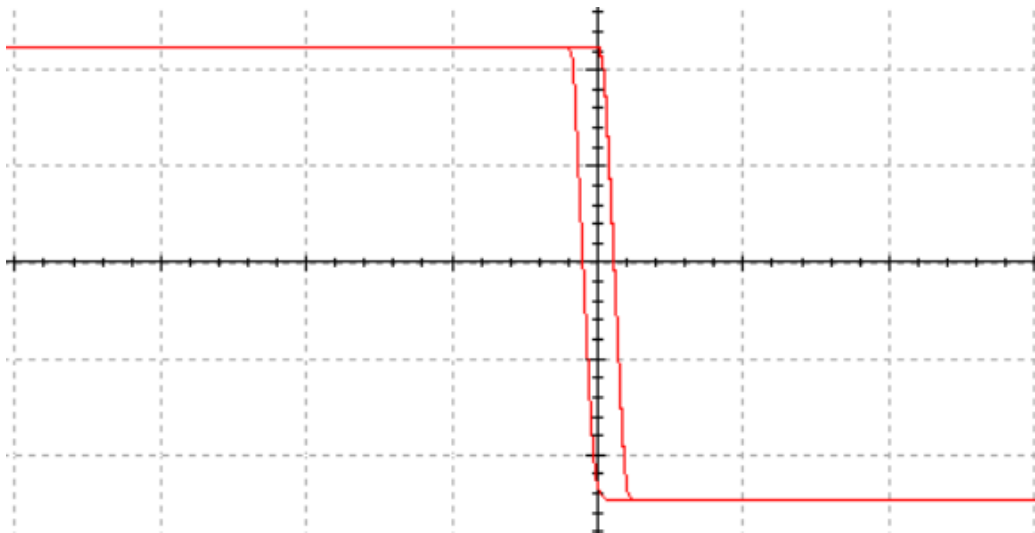

**Graph 2.4:** Transfer characteristics for a zero-crossing detector circuit using Op-Amp.

## Result:

In comparator circuit, for input sinusoidal signal, a digital signal with a positive peak of  $+V_{CC}$  and negative peak of  $-V_{CC}$  which intercepted the positive half cycle of input voltage at a reference voltage of 4.8V was found at the output.

**1801171**

In zero-crossing detector circuit, for input sinusoidal signal, a digital signal with  $-V_{CC}$  and  $V_{CC}$  peaks which crossed the input signal at zero voltage was obtained at the output.

**Conclusion:**